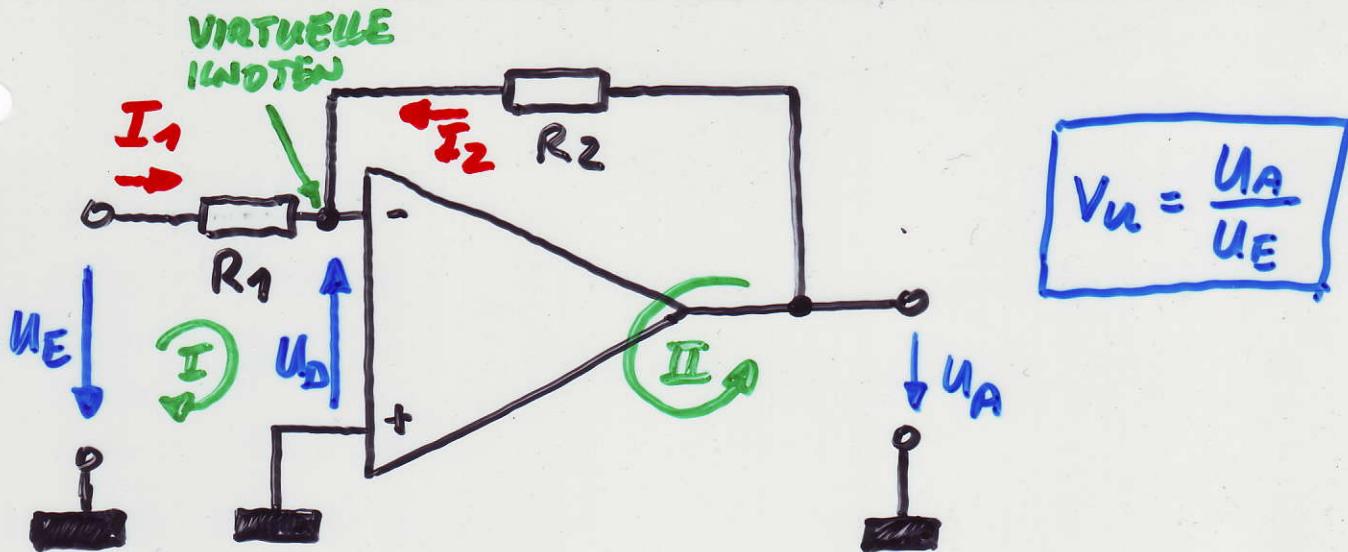


BETRIEBSVERSTÄRKUNG DES INVERTIERERS



\textcircled{I} = EINGANGSMASCHE

$$U_E = I_1 \cdot R_1 - U_D \quad U_D = \text{VERNACHLÄSSIGBAR} \\ \text{DA } I_D \text{ NUR } 75 \mu\text{A}$$

$$R_1 = \frac{U_E}{I_1} = R_{\text{EING.}}$$

\textcircled{II} = AUSGANGSMASCHE

$$U_A = I_2 \cdot R_2 - U_D$$

VIRTUELLE KNOTEN

$$I_1 + I_2 + I_D = 0 \Rightarrow I_1 = -I_2$$

$$I_1 = \frac{U_E}{R_1} ; \quad I_2 = \frac{U_A}{R_2}$$

$$\frac{U_E}{R_1} = - \frac{U_A}{R_2}$$

$$V_u = \frac{U_A}{U_E} = - \frac{R_2}{R_1}$$